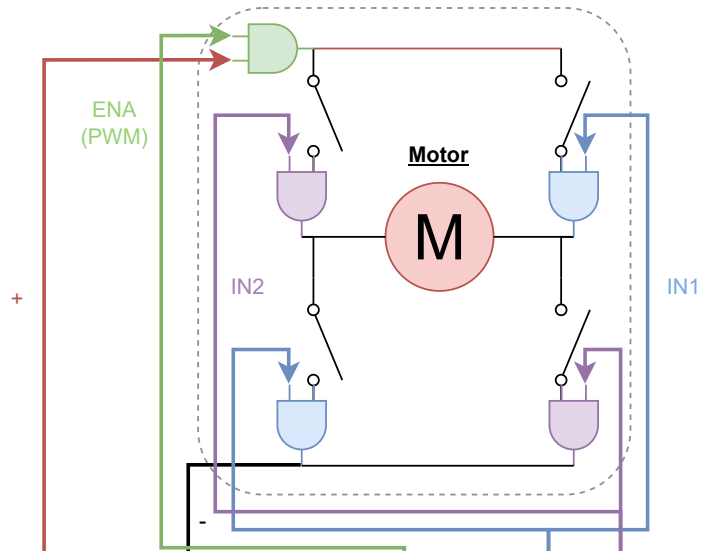


### H-Bridge (Motor Driver)



\* 3.3v logic high used, with internal pull-up, to read HIGH on a complete circuit

### Hinge-Arm Switch

